

Asadullah Jamalov

FET Amplifiers Tutorial 4

$$1) I_D = I_{DSS} \cdot \left(1 - \frac{I_D \cdot R_S}{V_{GS(off)}} \right)^2 ; V_{GS} = -I_D \cdot R_S$$

$$I_D = 4.3 \cdot 10^{-3} \cdot \left(1 - 2 \cdot \frac{I_D \cdot 1.1 \cdot 10^3}{7.7} + \frac{I_D^2 \cdot 1.1^2 \cdot 10^6}{7.7^2} \right)$$

$$I_D = 4.3 \cdot 10^{-3} - 1.23 I_D + 87.76 I_D^2$$

$$87.76 I_D^2 - 2.23 I_D + 4.3 \cdot 10^{-3} = 0 \Rightarrow I_D = 2.1 \text{ mA}$$

~~scribbles~~

$$V_{GS} = -I_D \cdot R_S = -2.31 \text{ V}$$

$$2) a) V_G = 0 \text{ V} ; V_S = 0 \text{ V}$$

$$V_D = V_{DD} - I_D R_D = 15 \text{ V} - 8 \text{ mA} \cdot 1 \text{ k}\Omega = 7 \text{ V}$$

$$b) V_G = 0 \text{ V}$$

$$V_S = -I_D R_D = -3 \text{ mA} \cdot 330 \Omega = -0.99 \text{ V}$$

$$V_D = -V_{DD} + I_D R_D = -10 \text{ V} + 3 \text{ mA} \cdot 1.5 \text{ k}\Omega = -5.5 \text{ V}$$

$$c) V_G = \left(\frac{R_2}{R_1 + R_2} \right) \cdot V_{DD} = 3.837 \text{ V}$$

$$V_S = 0 \text{ V}$$

$$V_D = V_{DD} - I_D R_D = 12 \text{ V} - 6 \text{ mA} \cdot 1 \text{ k}\Omega = 6 \text{ V}$$

$$3) \quad V_D = V_{DD} - I_D R_D = 12V - 2.83mA \cdot 1.5k\Omega = 4.455V$$

$$V_S = I_D R_S = 2.83V$$

$$V_{DS} = V_D - V_S = 4.455 - 2.83 = 4.925V$$

$$V_{GS} = V_G - V_S = 0V - 2.83V = -2.83V$$

$$4) \quad R_d = R_D \parallel R_L = \frac{1.5 \cdot 10}{11.5} = 1.304k\Omega$$

$$A_v = g_m \cdot R_d = 5000\mu S \cdot 1.304k\Omega = 6.52$$


$$V_{out(pp)} = 2\sqrt{2} \cdot 50mV \cdot 6.52 = 922mV$$

$$5) \quad a) \quad R_d = R_D \parallel R_L = \frac{1.2 \cdot 22}{23.2} = 1.14k\Omega$$


$$A_v = g_m \cdot R_d = 3.8mS \cdot 1.14k\Omega = 4.332$$

$$b) \quad R_d = R_D \parallel R_L = \frac{2.2 \cdot 10}{12.2} = 1.8k\Omega$$
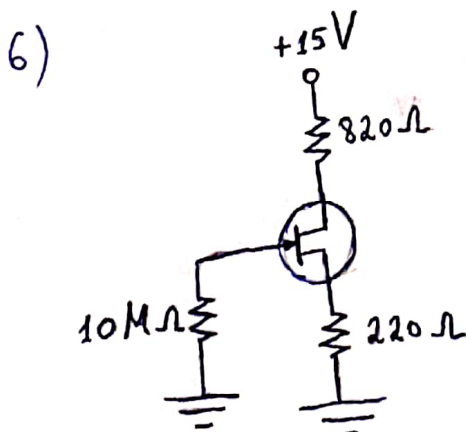
$$A_v = g_m \cdot R_d = 5.5mS \cdot 1.8k\Omega = 9.9$$



DC equivalent

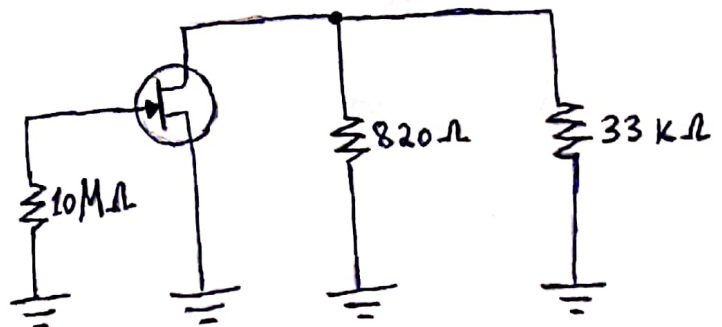

AC equivalent

$$7) R_L' = R_L \parallel 4.7 \text{ k}\Omega = \frac{3.3 \cdot 4.7}{8} = 1.939 \text{ k}\Omega$$

$$R_d = R_D \parallel R_L' = \frac{820 \cdot 1939}{2759} = 576.29 \Omega$$

$$A_v = g_m \cdot R_d = 4.41 \text{ mS} \cdot 576.29 \Omega = 2.541$$

$$8) R_{in(\text{gate})} = \left| \frac{V_{GS}}{I_{GSS}} \right| = \left| \frac{-15 \text{ V}}{25 \text{ nA}} \right| = 600 \text{ M}\Omega$$

$$R_{in} = R_G \parallel R_{in(\text{gate})} = \frac{10 \cdot 600}{610} = 9.84 \text{ M}\Omega$$

$$9) R_s = R_S \parallel R_L = 1.2 \text{ k}\Omega \parallel 1 \text{ k}\Omega = \frac{1.2 \cdot 1}{2.2} = 0.545 \text{ k}\Omega$$

$$A_v = \frac{g_m \cdot R_s}{1 + g_m R_s} = \frac{5500 \mu\text{S} \cdot 545 \Omega}{1 + 5500 \mu\text{S} \cdot 545 \Omega} = 0.75$$

$$R_{IN(\text{gate})} = \left| \frac{V_{GS}}{I_{GSS}} \right| = \left| \frac{-15 \text{ V}}{50 \text{ pA}} \right| = 3 \cdot 10^{11} \Omega$$

$$R_{in} = R_G \parallel R_{IN(\text{gate})} = 10 \text{ M}\Omega \parallel 3 \cdot 10^{11} \Omega \approx 10 \text{ M}\Omega$$

$$10) A_v = g_m \cdot R_d = 3500 \mu\text{S} \cdot 10 \text{ k}\Omega = 35$$

$$R_{in} = \left(\frac{1}{g_m} \right) \parallel R_s = \left(\frac{1}{3500 \mu\text{S}} \right) \parallel 2.2 \text{ k}\Omega = \frac{285.7 \Omega \cdot 2200 \Omega}{2485.7 \Omega} =$$

$$= 252.86 \Omega$$

$$11) R_d = R_{D2} \parallel R_L = \frac{10 \text{ k}\Omega \cdot 10 \text{ k}\Omega}{20 \text{ k}\Omega} = 5 \text{ k}\Omega$$

$$A_v = g_m \cdot R_d = 2000 \mu\text{S} \cdot 5 \text{ k}\Omega = 10$$

$$R_{in(\text{source})} = \frac{1}{g_m} = \frac{1}{2000 \mu\text{S}} = 500 \Omega$$

$$R_{in} = R_{in(\text{source})} \parallel R_s = \frac{500 \Omega \cdot 4700 \Omega}{5200 \Omega} = 451.9 \Omega$$

- V_{DD} is negative, because it is p-channel JFET
- Given semiconductor device is JFET transistor.

(2)

V_A	V_B	Q_1	Q_2	Q_3	Q_4	V_{out}
0	0	on	off	off	on	V_{DD}
0	V_{DD}	off	off	off	on	V_{DD}
V_{DD}	0	on	off	off	off	V_{DD}
V_{DD}	V_{DD}	off	on	on	off	0

(3)

V_A	V_B	Q_1	Q_2	Q_3	Q_4	V_{out}
0	0	on	off	on	off	V_{DD}
0	V_{DD}	off	on	on	off	0
V_{DD}	0	on	off	on	off	0
V_{DD}	V_{DD}	off	on	off	on	0

- 14) When the input pulse is at V_{DD} , Q_1 is off and Q_2 is on, connecting output to GND.
 When the input pulse is at 0, Q_1 is on and Q_2 is off, connecting output to V_{DD}

