



Analog Electronics

FET Amplifiers

Tutorial 4

The Common-Source Amplifier

1. Determine I_D and V_{GS} at the Q point for the JFET amplifier in Figure 1. The typical I_{DSS} for this particular JFET is 4.3 mA and $V_{GS(off)}$ is -7.7 V. [5 marks]

 


Figure 1

2. Calculate the dc voltages from each terminal to ground for the FETs in Figure 2. [5 marks]

 


Figure 2

3. Given that $I_D = 2.83$ mA in Figure 3, find V_{DS} and V_{GS} . $V_{GS(off)} = -7$ V and $I_{DSS} = 8$ mA. [4 marks]

 


Figure 3



4. If a 50 mV rms input signal is applied to the amplifier in Figure 3, what is the peak to peak output voltage? $g_m = 5000 \mu S$. [5 marks]
5. Determine the voltage gain of each common-source amplifier in Figure 4. [8 marks]

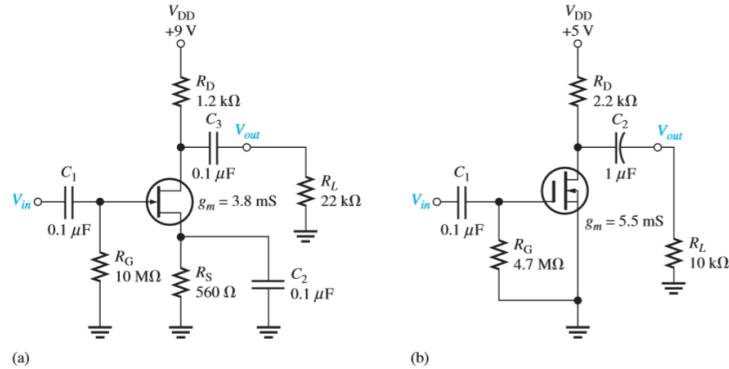


Figure 4

6. Draw the dc and ac equivalent circuits for the amplifier in Figure 5. [4 marks]

 


Figure 5

7. A resistor 4.7 kΩ is connected in parallel with R_L in Figure 5. What is the voltage gain? $g_m = 4.41 \text{ mS}$ [5 marks]
8. What input resistance is seen by the signal source? $I_{GSS} = 25 \text{ nA}$, $V_{GS} = -15 \text{ V}$. [8 marks]

 


Figure 6



The Common Drain Amplifier

9. For the source follower in Figure 7, determine the voltage gain and input resistance, $I_{GSS} = 50 \text{ pA}$ at $V_{GS} = -15 \text{ V}$ and $g_m = 5500 \text{ }\mu\text{S}$. [15 marks]

 


Figure 7



The Common Gate Amplifier

10. Determine the voltage gain and input resistance of the common-gate amplifier in Figure 8. [8 marks]

 


Figure 8

11. Common gate amplifier [12 marks]

- Determine the minimum voltage gain and input resistance of amplifier in Figure 9, given that $g_m=2000 \mu\text{S}$, $I_{GSS} = 5 \text{ nA}$, $V_{GS} = 20 \text{ V}$.
- Why V_{DD} is negative?
- What is the type of given semiconductor device?

 


Figure 9



12. NAND gate is created by using MOSFETs. Gate consists of 2 inputs and an output. According to the Figure 10, fill the given table. [8 marks]

V_A	V_B	Q_1	Q_2	Q_3	Q_4	V_{out}
0	0					
0	V_{DD}					
V_{DD}	0					
V_{DD}	V_{DD}					

 


Figure 10

13. Fill the table, in case, previous gate is replaced with NOR gate. [8 marks]

V_A	V_B	Q_1	Q_2	Q_3	Q_4	V_{out}
0	0					
0	V_{DD}					
V_{DD}	0					
V_{DD}	V_{DD}					

 


Figure 11

14. A pulse waveform is applied to a CMOS inverter as shown in Figure 12. Determine the output waveform and explain the operation. [5 marks]

 


Figure 12